


National University of Computer and Emerging Sciences, Lahore Campus

| | | | | |
|---|--------------|-----------------------|--------------|-----------|
|  | Course Name: | Computer Architecture | Course Code: | EE204 |
| | Program: | BS(Computer Science) | Semester: | Fall 2019 |
| | Duration: | 30 Minutes | Total Marks: | 20 |
| | Paper Date: | 16-09-2019 | Weight | ~3 |
| | Exam Type: | Quiz 1d | Page(s): | 2 |

Student : Name: _____ **Roll No.** _____
Section: _____

Question 1 a [8]

Using four bit number, multiply 11×6 using original multiplier circuit (without optimization) discussed in the class. Value of each register is initialized in the table below. List different steps that will be performed in each iteration and the resulting value of each register.

| Iteration | Step | Multiplier | Multiplicand | Product |
|-----------|----------------|------------|--------------|----------|
| 0 | Initial values | 0110 | 00001011 | 00000000 |
| 1 | | | | |
| 2 | | | | |
| 3 | | | | |
| 4 | | | | |

Question 1 b [4]

Bits have no inherent meaning. Given the bit pattern
0000 0000 0011 0110 0010 1000 0000 0010

- Assuming it as a MIPS instruction identify source and destination register numbers.
- Assuming it as a signed binary value, what is the corresponding integer value?

Question 2 [8]

| Input | Present State | | Next state | |
|-------|----------------|----------------|------------------|------------------|
| x | A _i | B _i | A _{i+1} | B _{i+1} |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 |

The state table shows the transitions of a sequential circuit with two memory elements.

- Write down the Boolean expressions describing the next state.
- Draw the circuit using the expressions.