

**Computer Architecture (EE 204)**

**Assignment # 1,**

**Total marks 70.**

**Due Date: 16 – 09 -2016**

**Plagiarism policy: All the students involved will be awarded zero in the first instance.  
You need to submit hardcopy. Please show your work clearly.**

**Assignment Description:**

Assignment covers concepts related to Arithmetic Micro-operations, Logic Micro-operations, Shift Micro-operations and Arithmetic Logic Shift Unit.

**Question1: Number Representations**

**(10 marks)**

- a) Convert  $(234.125)_{10}$  to Binary.
- b) What is the minimum number of bit needed to represent -145 in 2's complement signed representations?
- c) Write down 2's complement signed representation of -115 using 8 bits
- d) Perform the addition of following 8-bit signed binary numbers
  - i. 01110101
  - ii. 11011011
- e) Perform the subtraction of following unsigned decimal numbers  
 $10110 - 10010$

**Question2: Convert the following to 32-bit floating point representations.**

**(3+3+1+1+1+1 marks)**

- i. 300.375
- ii. -20.0
- iii. +inf
- iv. -inf
- v. 0
- vi. NAN

**Question3: The 8 bit registers, AR, BR, CR, and DR initially have the following values.**

AR = 11101011

BR = 10110011

CR = 11010000

DR = 10101010

**Determine the 8 bit values in each register after the execution of the following sequence of micro operations.**

**(10 marks)**

$CR \leftarrow \text{cil } CR$   
 $AR \leftarrow \text{ashl } AR$   
 $CR \leftarrow CR + DR, \quad BR \leftarrow \text{shl } BR$   
 $AR \leftarrow AR - CR$   
 $AR \leftarrow AR \wedge BR$

**Question 4: Circuit Design**

**(15 marks)**

A sequential circuit has two D flip-flops, A and B, maintaining state, two inputs X and Y and one output Z. The output and next flip-flop states are given by the equations.

$$\begin{aligned}
 A_{i+1} &= \bar{X}Y + XB_i \\
 B_{i+1} &= \bar{X}B_i + XA_i \\
 Z &= A_i(X + Y\bar{B}_i)
 \end{aligned}$$

- a) Draw the logic diagram of the circuit.
- b) Tabulate the state table
- c) Draw state diagram

**Note:** State table is similar to Truth Table but in this case, you determine the next state based on present state. For reference, you can see table 1-4 in chapter-1 on page 32.

**Question 5:**

**(10 marks)**

Design 2-bit binary counter using JK flip flops which supports parallel load and circular right shift as well. Clearly state the input required to trigger each input.

**Question 6: Design a 4-bit ALU that supports the following operations:**

**(15 marks)**

- 1)  $A + B$
- 2)  $A - B$  (2's complement subtraction)
- 3) 1-bit right shift (apply to input A)
- 4) 2-bit right shift (apply to input B)
- 5) 1-bit left shift (apply to input A)
- 6) 2-bit left shift (apply to input B)
- 7)  $A \& B$  (bitwise AND)
- 8)  $A | B$  (bitwise OR)